

# Diodes

Simple two-terminal electronic devices.

Made of semiconducting materials: silicon, gallium arsenide, indium phosphide, gallium nitride, etc. (EE 332 stuff.)

Semiconductors are interesting because their electrical properties can be varied over many order of magnitude: resistivity as high as  $10^7 \Omega\text{-m}$  (almost an insulator) or as low as  $10^{-6} \Omega\text{-m}$  (almost a conductor).

Also, semiconductors can be made in two different “varieties”: either *n-type* in which current is carried by electrons (as usual) or *p-type* which current is carried by positive charges called holes.

A diode consists of a p-type layer of semiconductor joined to a n-type layer, and so is also known as a *p-n junction*. Current flowing across this junction exhibits a very asymmetric, non-linear i-v characteristic.

The non-linearity will force us to change the way we analyze circuits.



# Diode applications

- Rectification – cutting off the top half or bottom half of a voltage signal.
- Voltage regulation – providing a steady voltage reference in a circuit.
- light-emitting diodes – for indicators
- light-emitting diodes – for illumination
- lasers - DVD players, fiber-optic communication, surgery
- photodetectors – sense presence of light, especially low levels or fast pulses
- photovoltaics (solar cells) – “green” electrical power generation
- building block for transistors






rectifying diode  
(switching or  
*small-signal*)

made of silicon



LEDs – various materials (not silicon).  
Different material = different colors.

laser

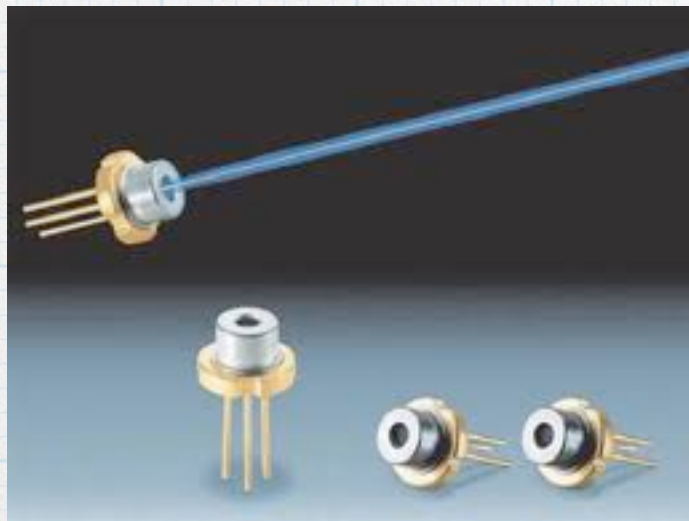




solar cell



LED lighting – usually gallium nitride  
(UV light) that excites a phosphor.



# Diode

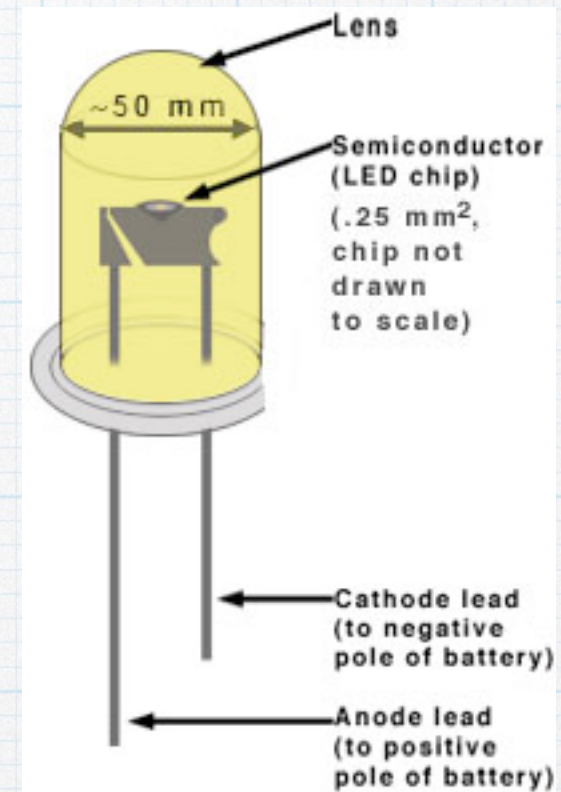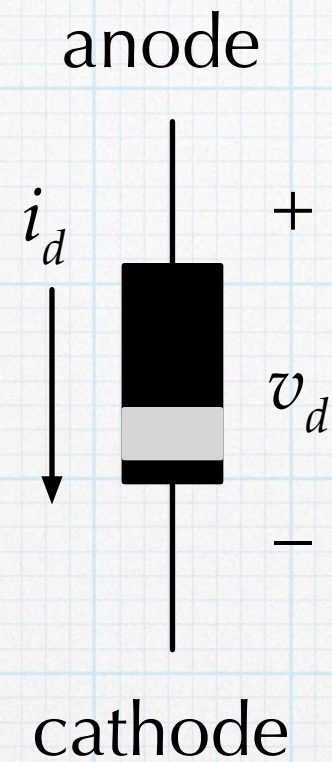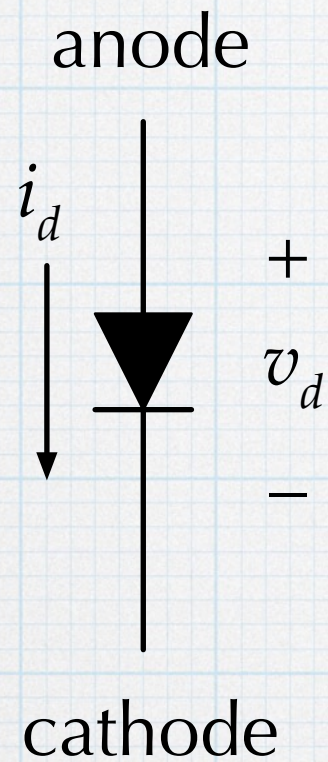


think “funnel” – it flows in one direction


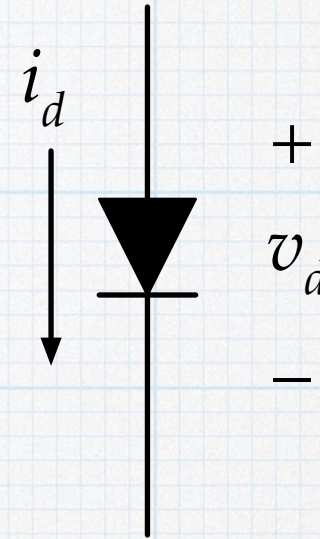
# diode i-v characteristic

ideal diode equation

$$i_D = I_S \left[ \exp \left( \frac{v_D}{kT/q} \right) - 1 \right]$$



Extremely non-linear. Will cause lots of problems in analyzing, but offers many opportunities for applications.

$I_S$  is a parameter of the diode, known as *saturation current* or *scale current*. Different for every diode. (Like  $R$  for a resistor.)

Typical:  $I_S \approx 10^{-14}$  A.

$kT$  is the thermal energy.  $k$  (Boltzmann's constant =  $1.38 \times 10^{-23}$  J/K),  $T$  = temperature in kelvin (K).


$q$  is the charge on one electron;  $kT/q$  is the thermal voltage.

At 300K (= 27°C, approximately room temperature),  $kT/q = 25.8$  mV.


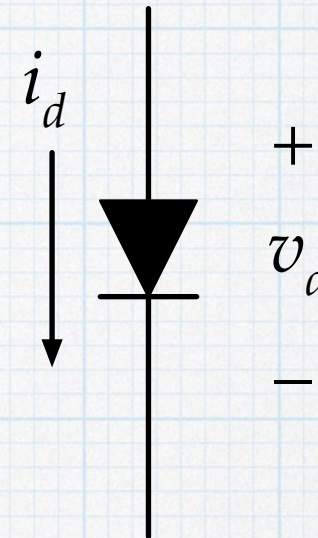
# diode: forward and reverse conduction

$$i_D = I_S \left[ \exp \left( \frac{v_D}{kT/q} \right) - 1 \right]$$



If  $v_D$  is positive,  $v_D \gg kT/q$ .

$$i_D \approx I_S \exp \left( \frac{v_D}{kT/q} \right)$$

Lots of current can flow. Increases rapidly as  $v_D$  increases. Forward *bias* or forward conduction.



If  $v_D$  is negative.

$$i_D \approx -I_S$$

A very small trickle of current flows, almost zero. Independent of the voltage. Reverse bias or reverse conduction.

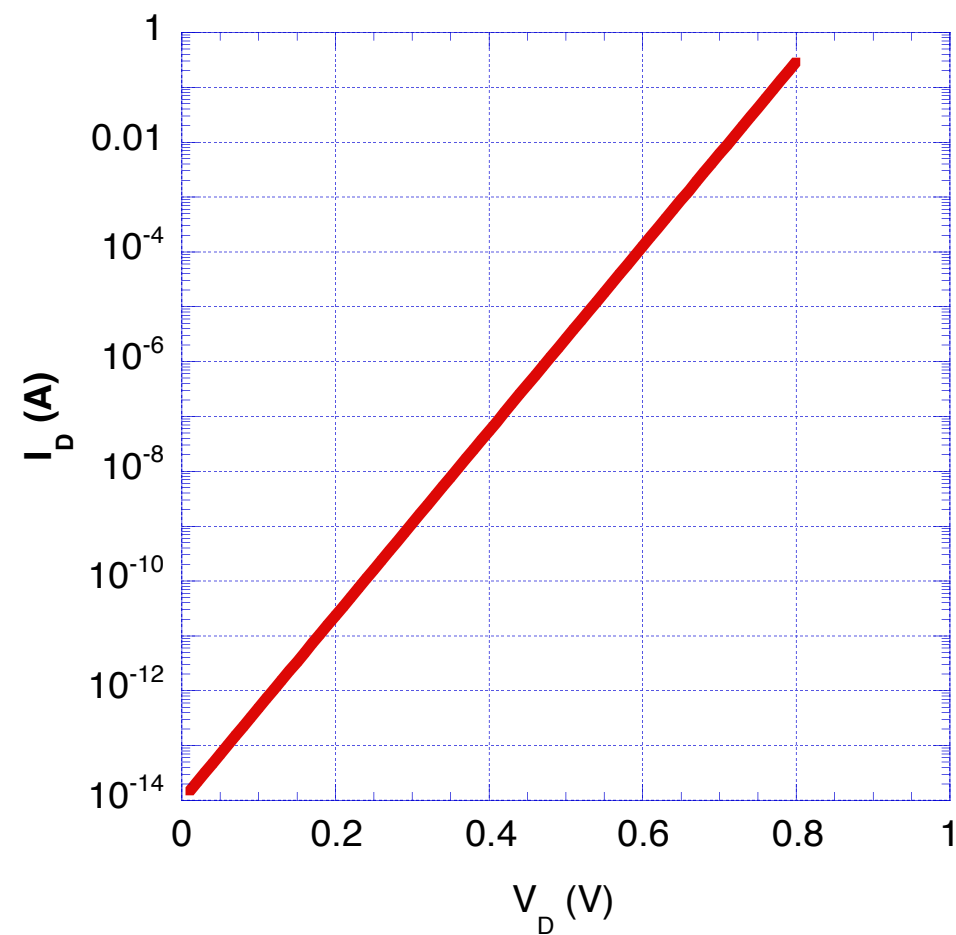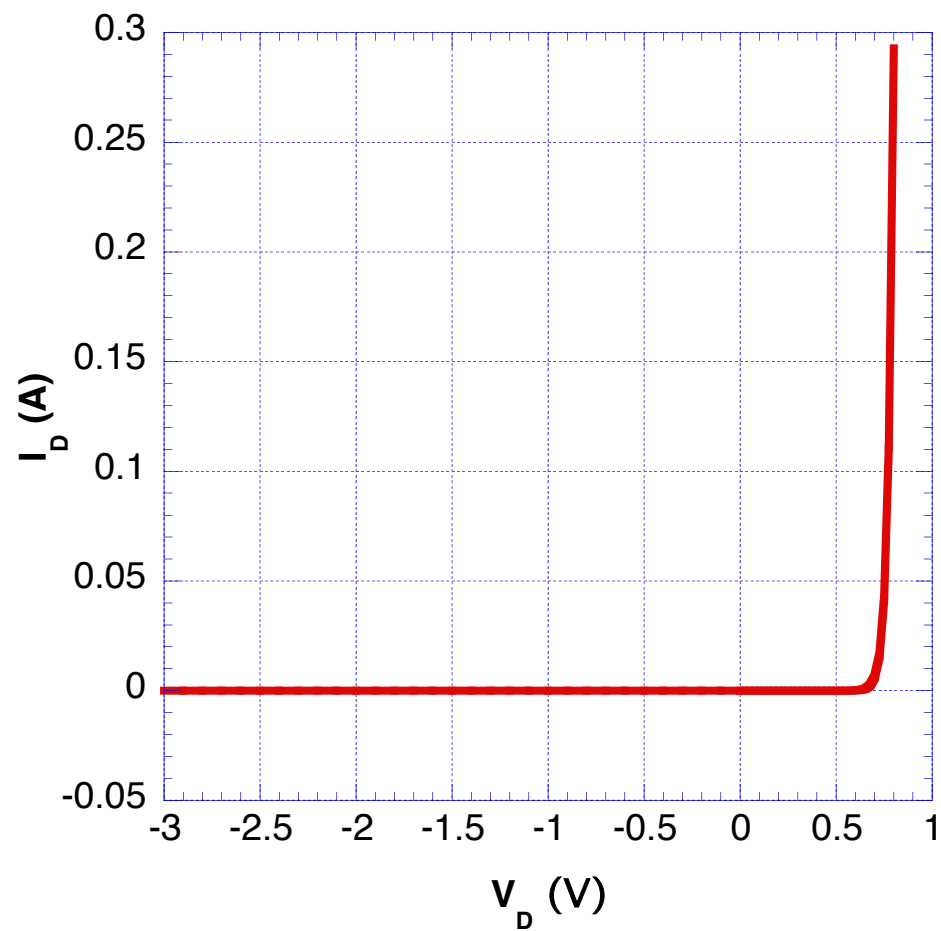The asymmetry between forward and reverse conduction is the basis for rectification – current can flow only one way (essentially). (Again, think funnel.)





Diode  $i$ - $v$   
 $I_S = 10^{-14}$  A  
 $T = 300$  K

Same diode  
 Forward voltage only  
 semi-log plot



# diodes in circuit

The non-linear behavior has some significant effects.

Basic notions are still valid: KCL and KVL, energy and power

Some techniques are invalid with non-linear elements: superposition, Thevenin.

Node-voltage and mesh-current techniques are still applicable, but the result is a set of non-linear equations, which are difficult to solve.


With non-linear elements, we will rely on:

- Approximating the device behavior with linear elements. This requires some guessing and then checking of the results. Of course, it is only approximate.
- SPICE


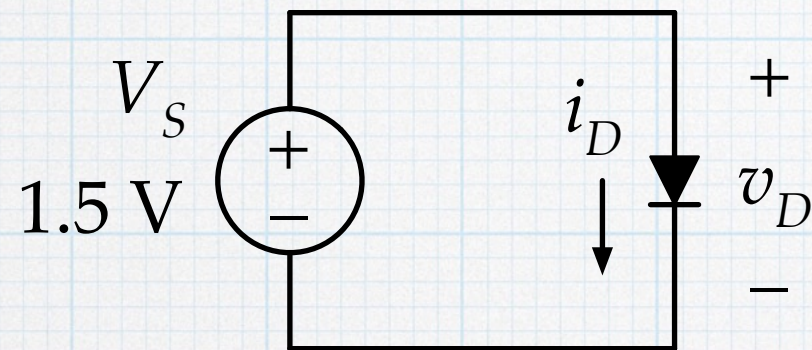
# diodes in circuits

Important: When working with diodes, don't EVER apply a forward voltage directly across the diode. The result is usually a dead diode.



$$I_S = 10^{-14} \text{ A}$$

$$\text{room temp: } kT/q = 25.8 \text{ mV.}$$


$$v_D = V_S$$

$$i_D \approx I_S \exp\left(\frac{v_D}{kT/q}\right)$$

$$= \left(10^{-14} \text{ A}\right) \exp\left(\frac{1.5\text{V}}{0.0258\text{V}}\right) = 1.8 \times 10^{+12} \text{ A}$$

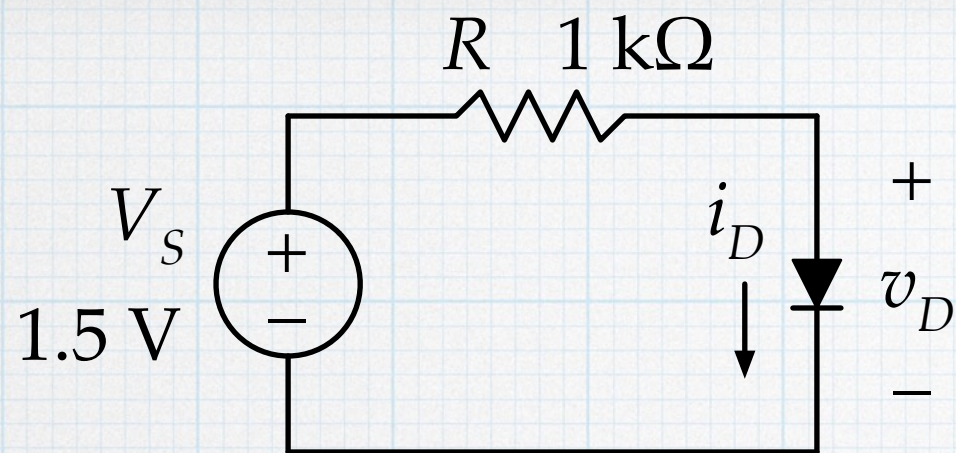This is absolutely absurd. Of course, what really happens is that the diode would burn up (due to instant heating) when the current hits 1 A or so. There must always be a current-limiting resistor in series.





$$I_S = 10^{-14} \text{ A}$$

$$\text{room temp: } kT/q = 25.8 \text{ mV.}$$

$$i_D = I_S \left[ \exp \left( \frac{v_D}{kT/q} \right) - 1 \right]$$

$$v_D = \frac{kT}{q} \ln \left( \frac{i_D}{I_S} + 1 \right)$$

$$V_S = v_R + v_D$$

$$V_S = i_D R + \frac{kT}{q} \ln \left( \frac{i_D}{I_S} + 1 \right)$$

??? Can't be solved in closed form.  
Transcendental equation. Must use  
iteration. (Trial-and-error.)

$$i_D = \frac{V_S}{R} - \frac{kT/q}{R} \ln \left( \frac{i_D}{I_S} + 1 \right) = 1.5 \text{ mA} - (0.0258 \text{ mA}) \ln \left( \frac{i_D}{10^{-11} \text{ mA}} + 1 \right)$$


1st guess

1.00 mA
0.846526 mA
0.850825 mA
0.850694 mA
0.850698 mA

$$i_D = 0.851 \text{ mA}$$

$$v_D = 0.649 \text{ V}$$



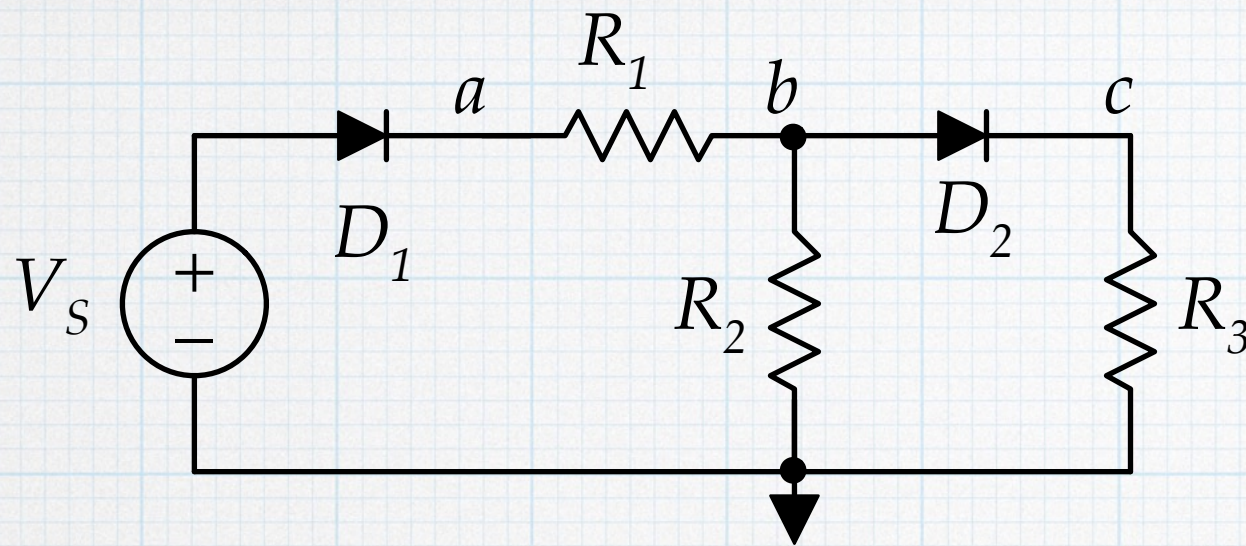

$$i_{D1} = \frac{v_a - v_b}{R_1}$$

$$v_{D1} = V_S - v_a$$

$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_2} + i_{D2}$$

$$v_{D2} = v_b - v_c$$

$$i_{D2} = \frac{v_c}{R_3}$$


$$I_{S1} \left[ \exp \left( \frac{V_S - v_a}{kT/q} \right) + 1 \right] = \frac{v_a - v_b}{R_1}$$

$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_2} + I_{S2} \left[ \exp \left( \frac{v_b - v_c}{kT/q} \right) + 1 \right]$$

$$I_{S2} \left[ \exp \left( \frac{v_b - v_c}{kT/q} \right) + 1 \right] = \frac{v_c}{R_3}$$

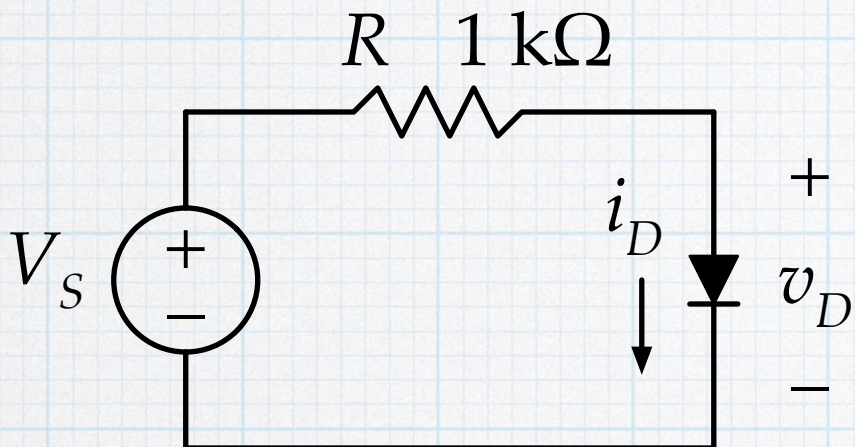3 non-linear equations in 3 unknowns  
Good luck with that!!





$$i_D = \frac{V_S}{R} - \frac{kT/q}{R} \ln \left( \frac{i_D}{I_S} + 1 \right)$$

When the diode is reverse-biased ( $V_S < 0$ , so  $v_D < 0$ ), the diode behaves essentially like an open circuit,  $i_D \approx 0$ .

When the diode is forward-biased ( $V_S > 0$ , so  $v_D > 0$ ), the diode voltage is roughly constant at 0.6 V - 0.7 V.

$V_S$ (V)	$v_D$ (V)	$i_D$ (mA)
-10	-10 V	$\approx 0$
-8	-8 V	$\approx 0$
-6	-6 V	$\approx 0$
-4	-4 V	$\approx 0$
-2	-2 V	$\approx 0$
0	0	0
1	0.628	0.372
2	0.661	1.339
3	0.6752	2.3248
4	0.6844	3.3156
5	0.6911	4.3088
6	0.6965	5.3035
7	0.701	6.299
8	0.7047	7.2953
9	0.708	8.292
10	0.711	9.289




# piecewise diode model


The results of the previous slide suggest the following approximate model.

- When the diode is reverse-biased, we can treat it as if it is an open-circuit
- When the diode is forward-biased, we treat it like an ideal source with a value of 0.7 V.

Reverse ( $v_D < 0$ )

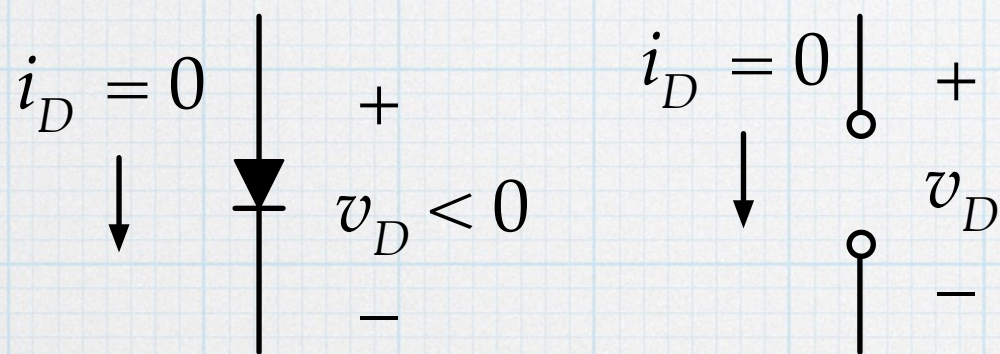

Forward ( $v_D > 0$ )

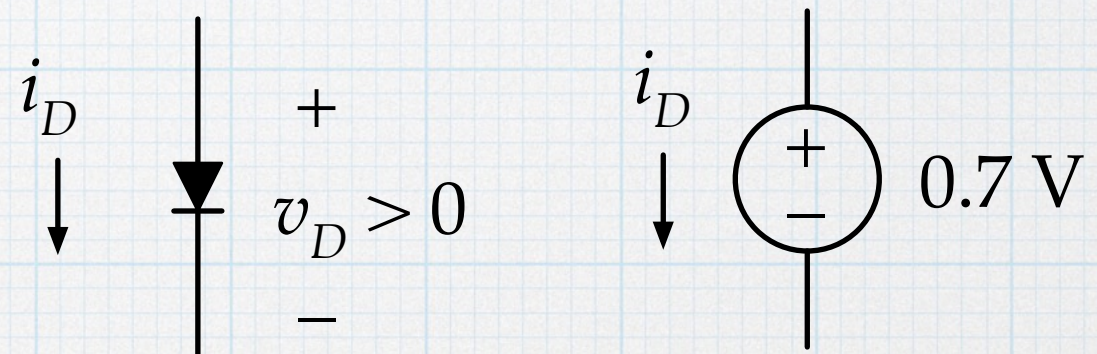


To use the models.


- Guess forward or reverse
- Insert the corresponding model
- Solve for voltage/current using model
- Check the result: for reverse,  $v_D < 0$ , for forward,  $i_D$  flows in correct direction

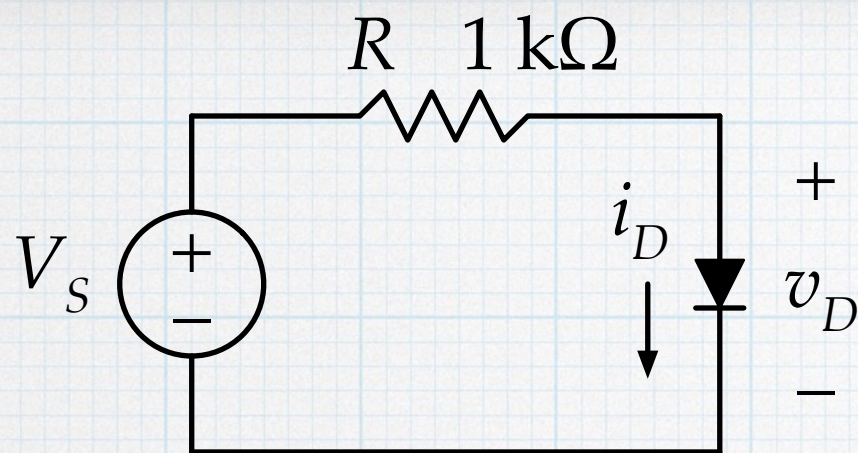Note that the diode is NOT a voltage source. It does not provide power to the circuit. It simply behaves as if it were a small voltage source or battery that is absorbing power.






Reverse ( $v_D < 0$  when  $V_S < 0$ )

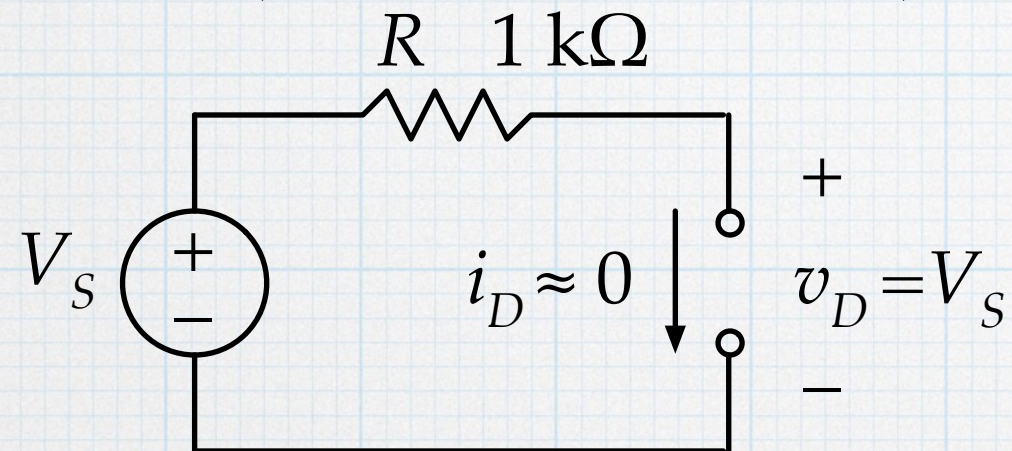

Forward ( $v_D > 0$  when  $V_S > 0$ )

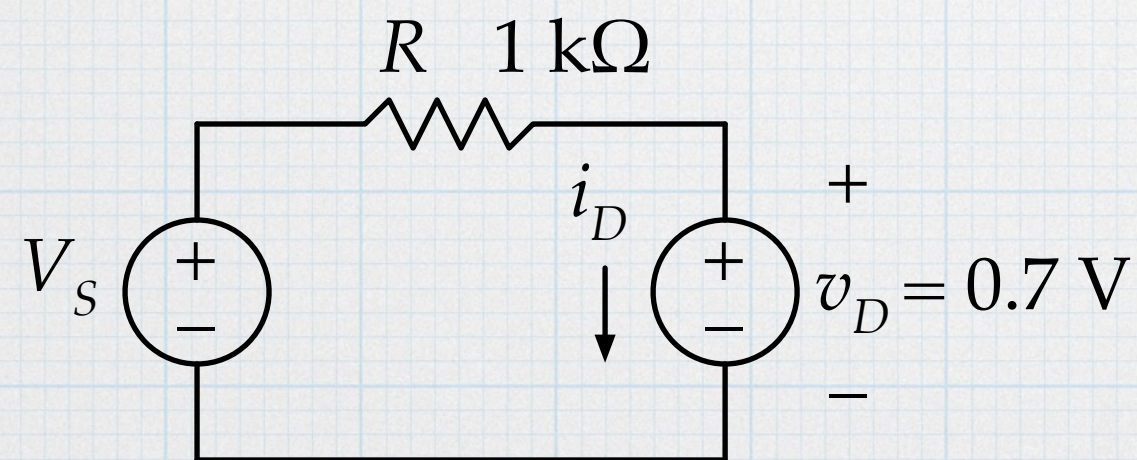


$$i_D = \frac{V_S - v_D}{R} = \frac{V_S - 0.7\text{V}}{R}$$

$V_S$ (V)	$v_D$ (V)	$i_D$ (mA)
-10	-10 V	$\approx 0$
-8	-8 V	$\approx 0$
-6	-6 V	$\approx 0$
-4	-4 V	$\approx 0$
-2	-2 V	$\approx 0$
0	0	0
1	0.7	0.3
2	0.7	1.3
3	0.7	2.3
4	0.7	3.3
5	0.7	4.3
6	0.7	5.3
7	0.7	6.3
8	0.7	7.3
9	0.7	8.3
10	0.7	9.3

compare to slide 12 – very similar



# Example

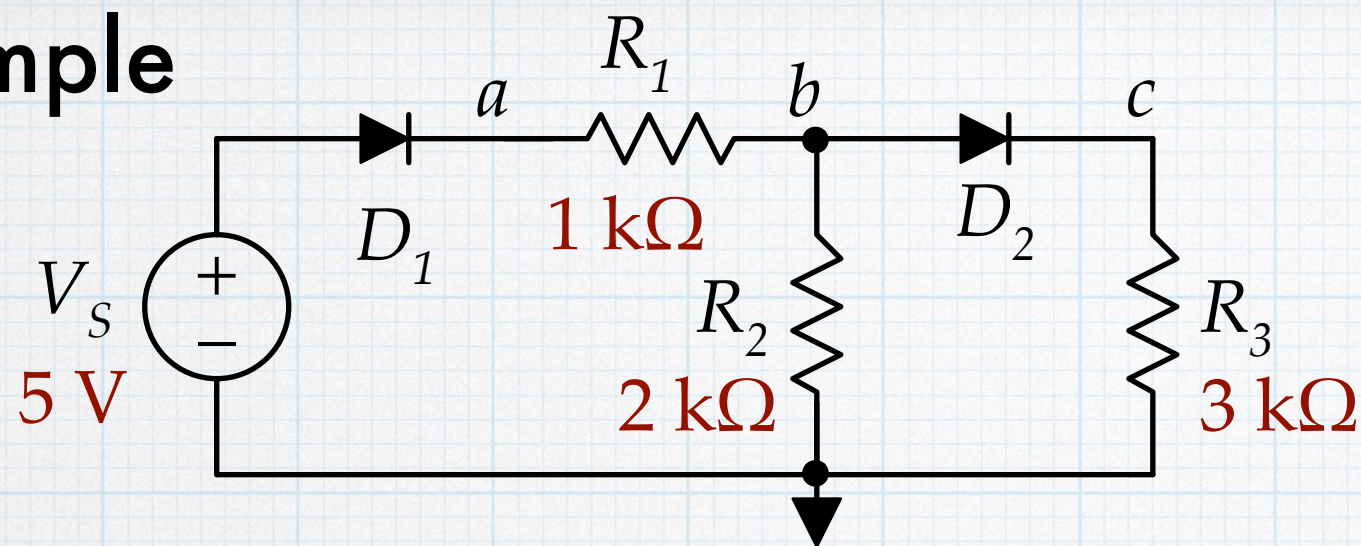

Since  $V_S$  is positive, we might guess that both diodes are forward-biased.

$$v_a = V_S - 0.7 \text{ V} = 4.3 \text{ V}.$$


$$v_c = v_b - 0.7 \text{ V}.$$

$$\frac{v_a - v_b}{R_1} = \frac{v_b}{R_2} + i_{D2}$$

$$i_{D2} = \frac{v_c}{R_3} = \frac{v_b - 0.7 \text{ V}}{R_3}$$

$$\frac{V_S - 0.7 \text{ V} - v_b}{R_1} = \frac{v_b}{R_2} + \frac{v_b - 0.7 \text{ V}}{R_3}$$

$$v_b = 2.47 \text{ V}.$$

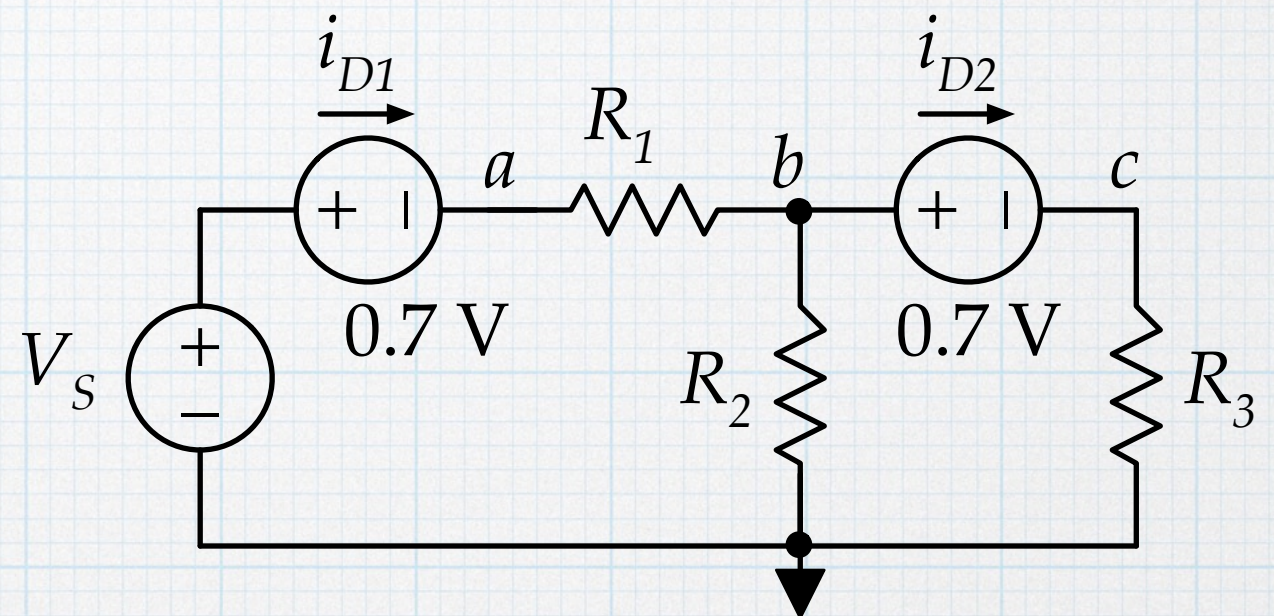

check:

$$i_{D1} = \frac{v_a - v_b}{R_1} = \frac{V_S - 0.7 \text{ V} - v_b}{R_1} = 1.83 \text{ mA}$$

$$i_{D2} = \frac{v_c}{R_3} = \frac{v_b - 0.7 \text{ V}}{R_3} = 0.591 \text{ mA}$$

Both currents are positive, consistent with forward conducting diodes. The guesses were correct.